



Scuttle robot Wiring Guide (rev 2020.11.10)

Important Info:


To match the beaglebone pins to the pin numbers on the diagram:

The tiny white circle on the silkscreen at each connector indicates “pin1”

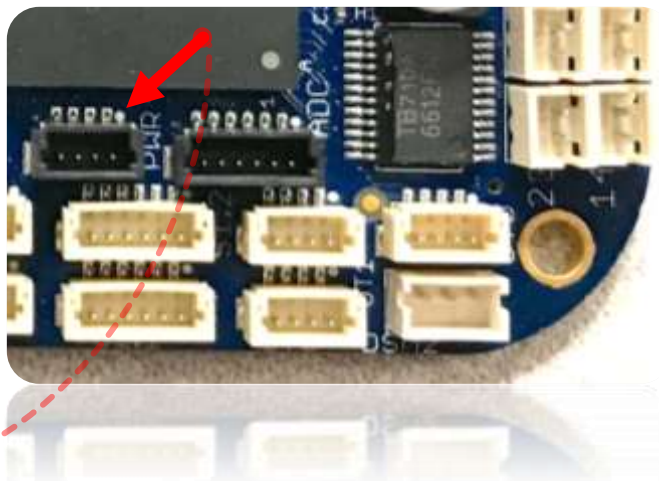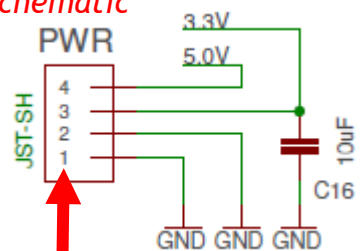All images of this style are copied directly from the beaglebone schematic



Verified Sensors & Actuators


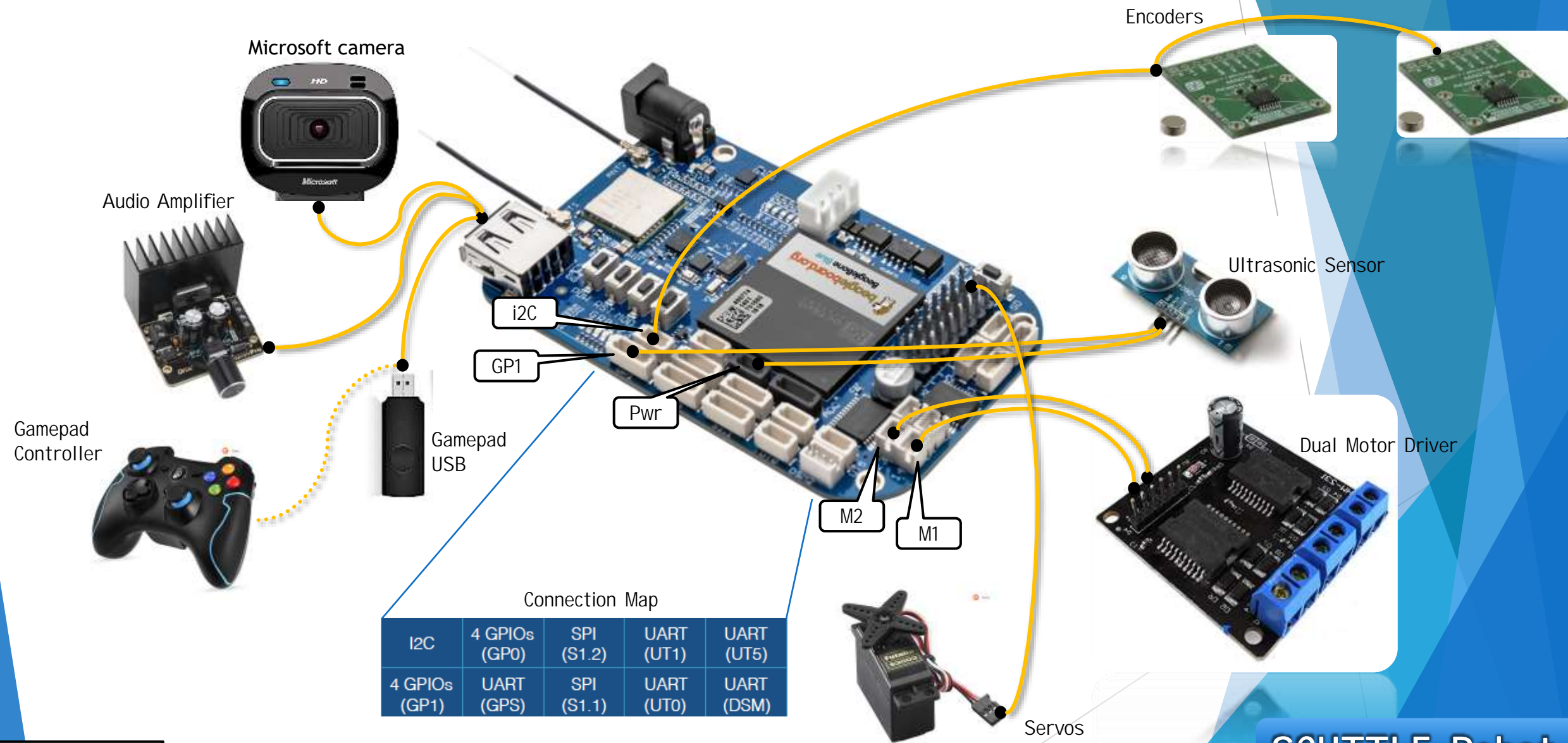


If you see a mistake email:
scuttleproject@gmail.com

SCUTTLE Robot

Motor Driver Signal Cables

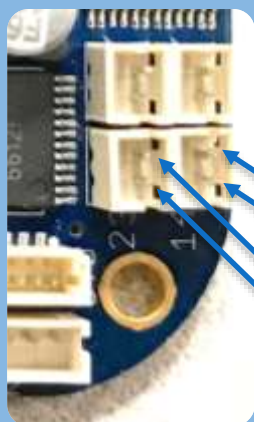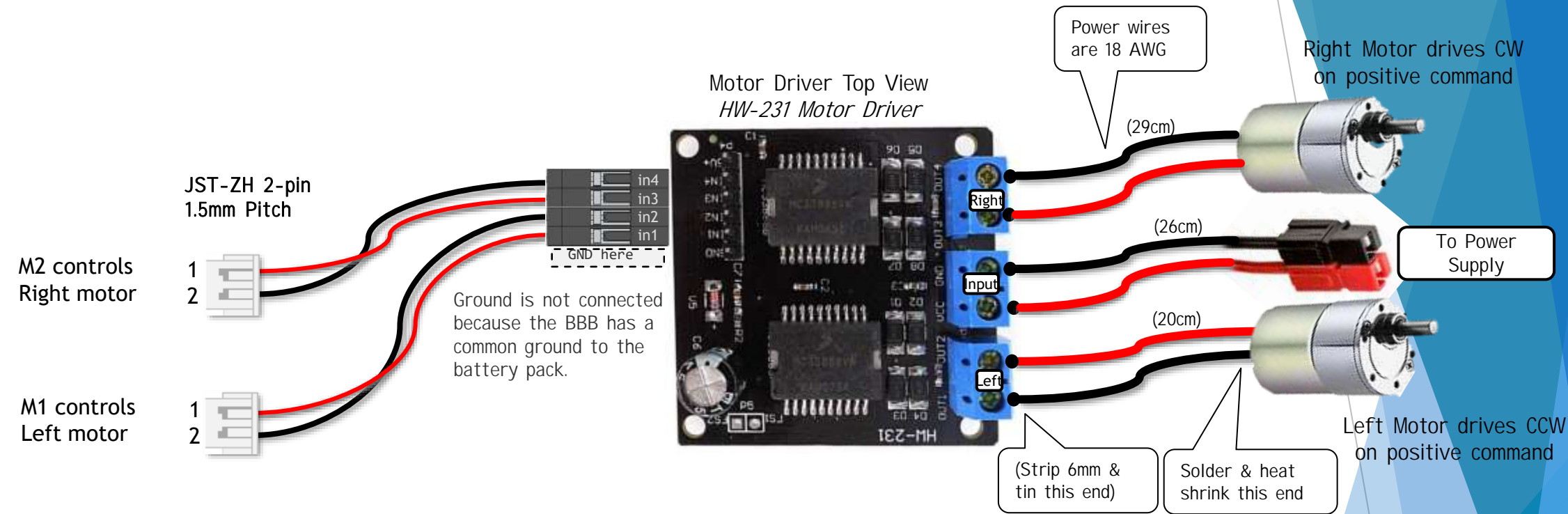If you see a mistake email:
scuttleproject@gmail.com




Pin 1 should be HIGH when
motor is driven FORWARD

Motor1 Pin1
Motor1 Pin2

Motor2 Pin1
Motor2 Pin2

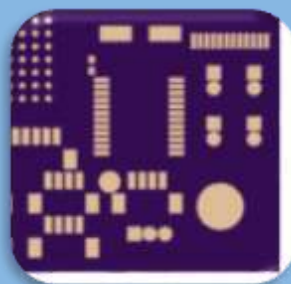Hardware design convention:
Pin 1 uses the square solder pad.



Connector vector
image reserved.




SCUTTLE Robot

H-Bridge L298N (optional)

If you see a mistake email:
scuttleproject@gmail.com

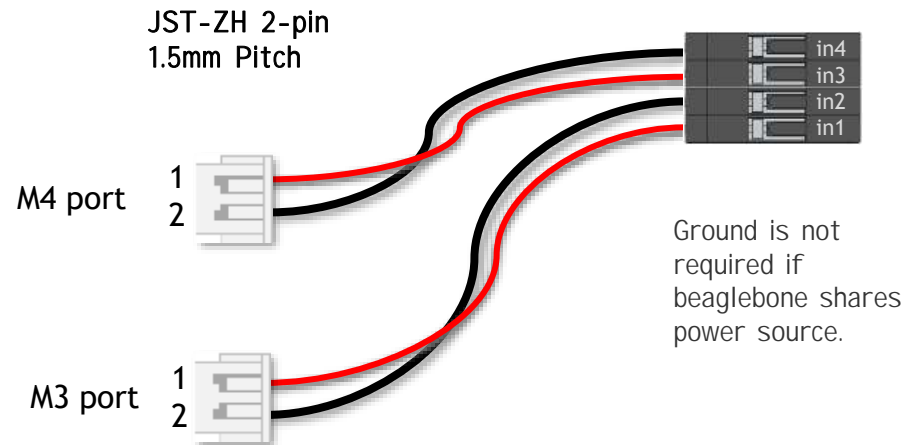A versatile and cheap device for delivering variable voltage to low-powered DC actuators.



L298N DUAL H-BRIDGE



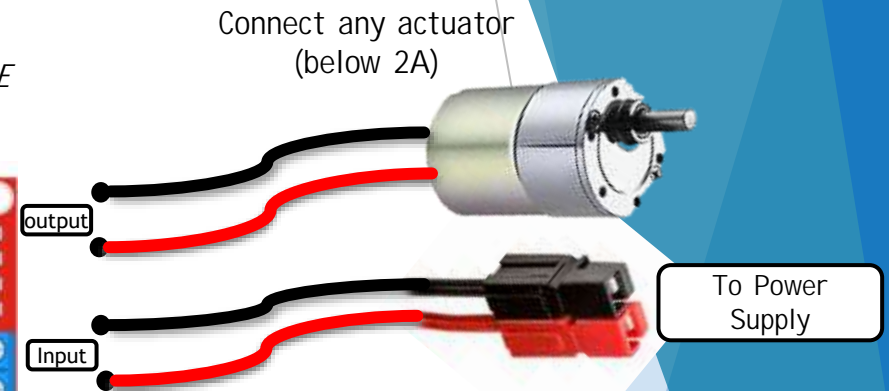


Image (and more great info!) found at LastMinutEngineers.com

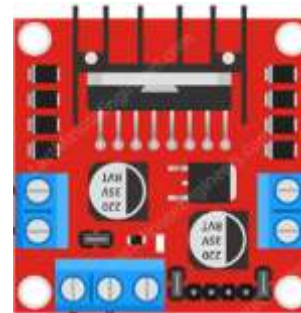



Pin 1 should be HIGH when
motor is driven FORWARD

Motor3 Pin1
Motor3 Pin2

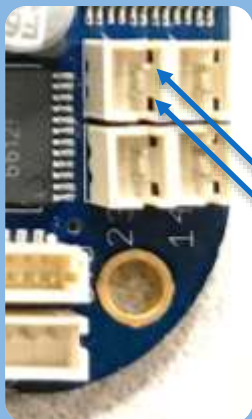


More information about the 5v regulator
Found on the datasheet ([L78M05](#))

Ultrasonic Distance Sensor (GPIO)

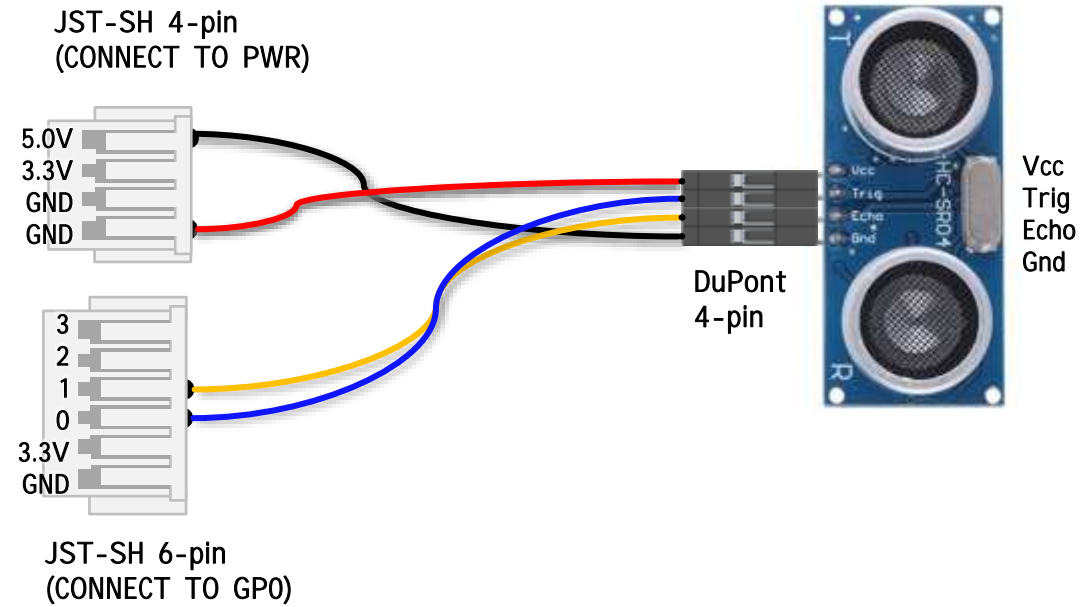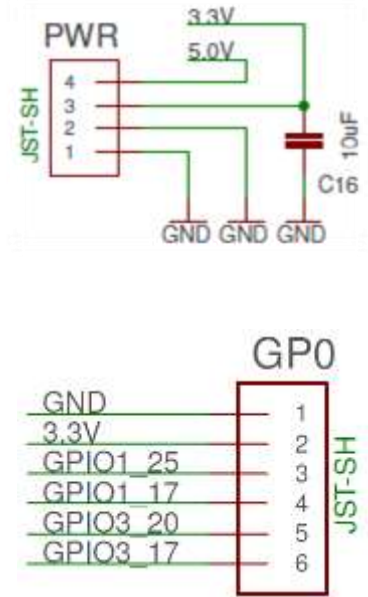

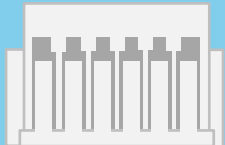
*NOTE: For JST connectors out-of-box,
the colors are not in the correct order.
You need to rearrange them.*



Beaglebone to I2C bus cable

Diagram

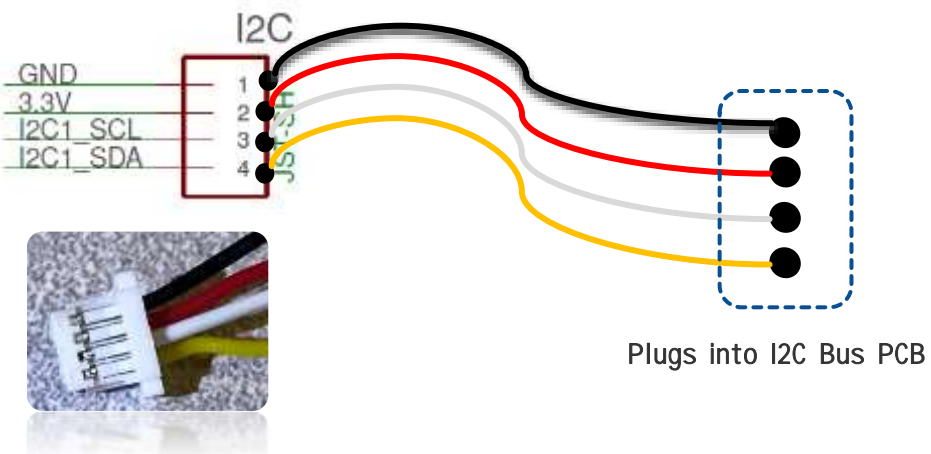BeagleBone I2C Connector
Style: JST-SH 4-pin




Cable Design

(I2C port on Beagle)
Style: JST-SH 4-pin




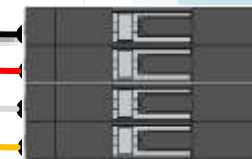DuPont style
2.54mm female 4-pin
(plugs into bus board)



Compass CMPS or CMPS2 (I2C)

Plugs Into I2C Bus Board


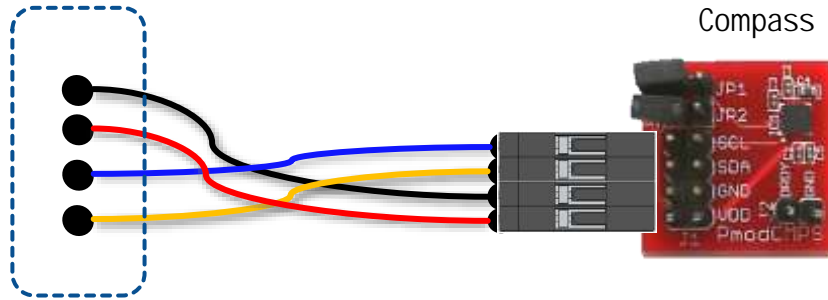


This compass is not necessary since you can access the compass on the beaglebone blue. Be sure to calibrate the compass on the blue since it lies within close proximity of magnetic hardware on the robot.



I2C Bus Board

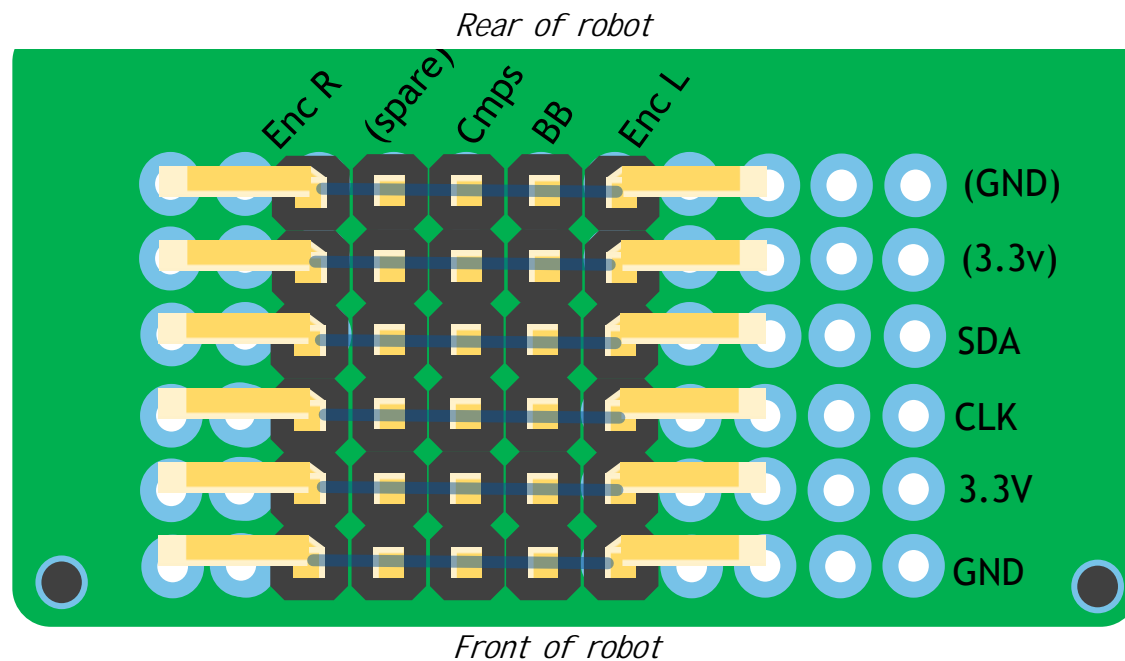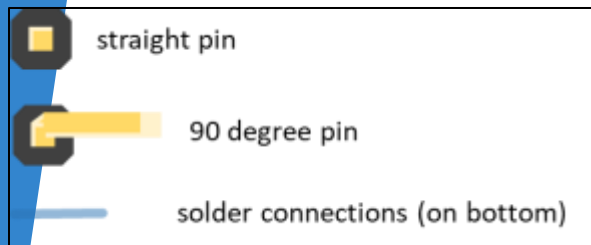
The board is made from a breadboard and soldered manually. The board can be cut between rows J & K. The solder bridges all pins from left to right.



Encoder AMS AS5048 (I2C)

Left Hand Encoder
A1 is pulled **down** to GND
I2C address is 0x40

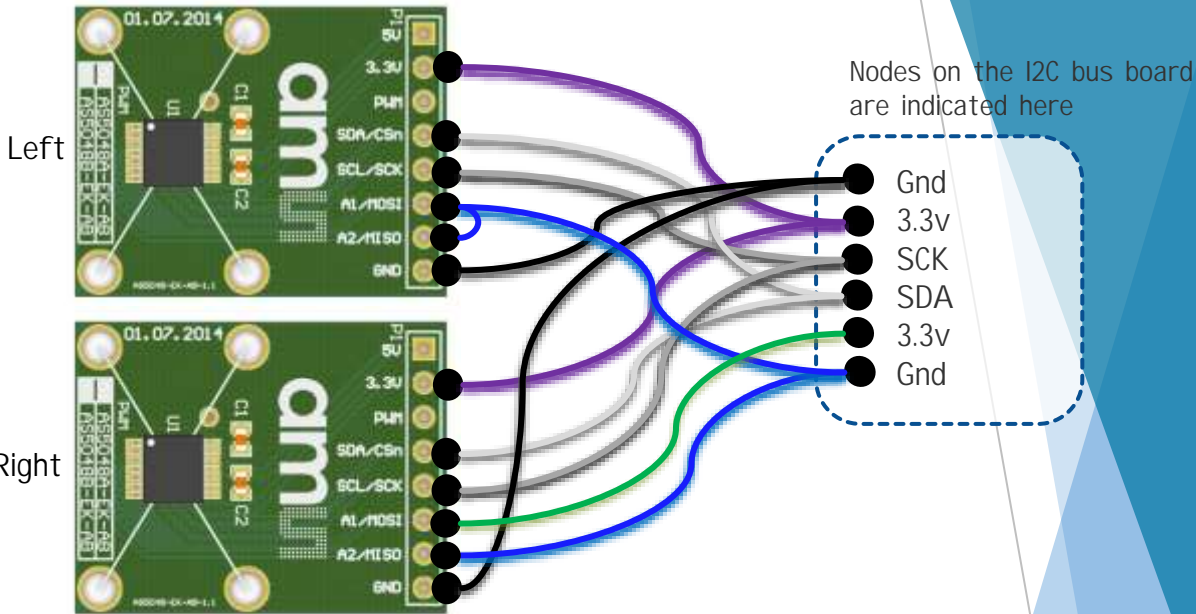
Right Hand Encoder
A1 is pulled **up** to 3.3v
I2C address is 0x41



PIN	Left	Right
A1	0 (low)	1 (high)
A2	0 (low)	0 (low)
i2C Address	0x40	0x41

On the Left Hand Encoder PCB, bridge the pins
A1 and A2 using solder, to each other.

Encoder Cables

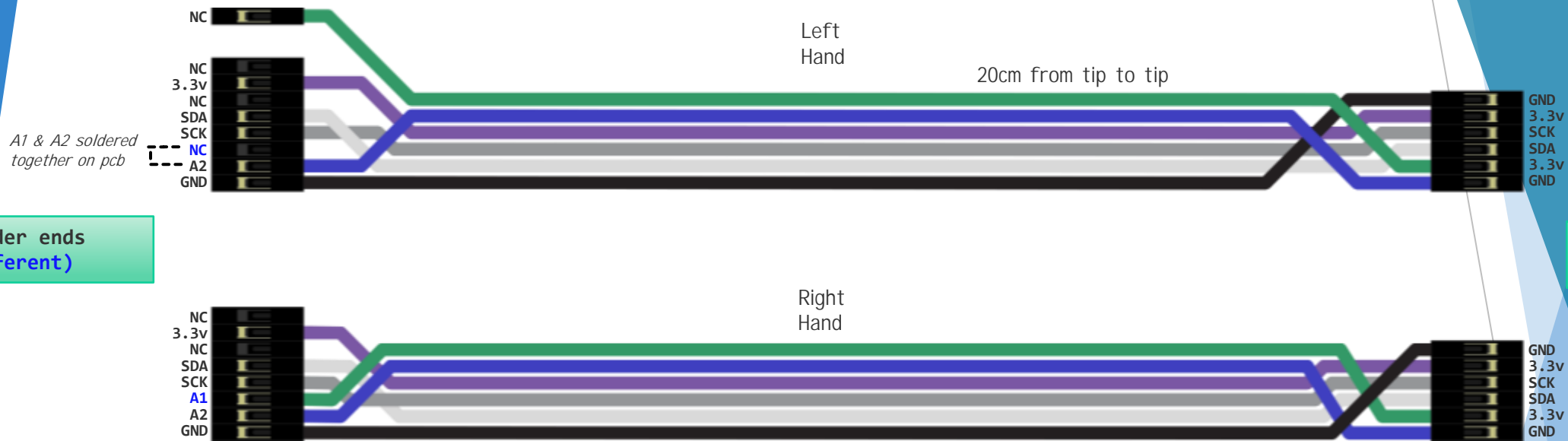


Encoder ends
(different)

Bus Board Ends
(matching)

Battery

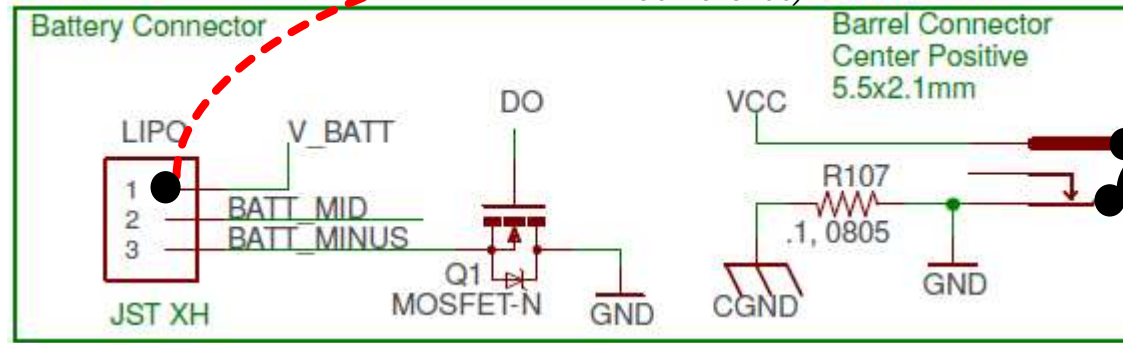*As an option, bridge
LiPo terminal to 12v
positive terminal (see
Servo Slide)*



The "Battery Connector" is disconnected. Actual battery uses Barrel Connector.




Connects to
battery Pack

Barrel Plug

Battery Pack (regular configuration)

Bottom Side

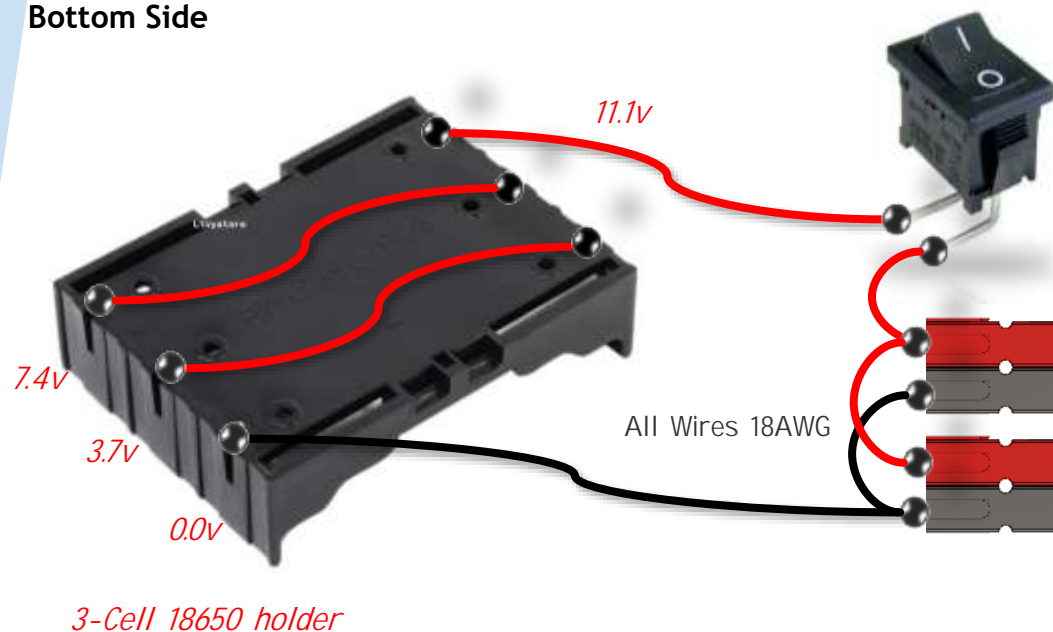

Switch PN:SRB22A2FBBNN
Carries 10A max

Two pairs of Anderson
connectors are attached here.

You may build a battery pack without a Battery Management System (BMS) as shown here, but our latest design includes BMS. See next slide.

Battery Pack (enhanced with BMS)

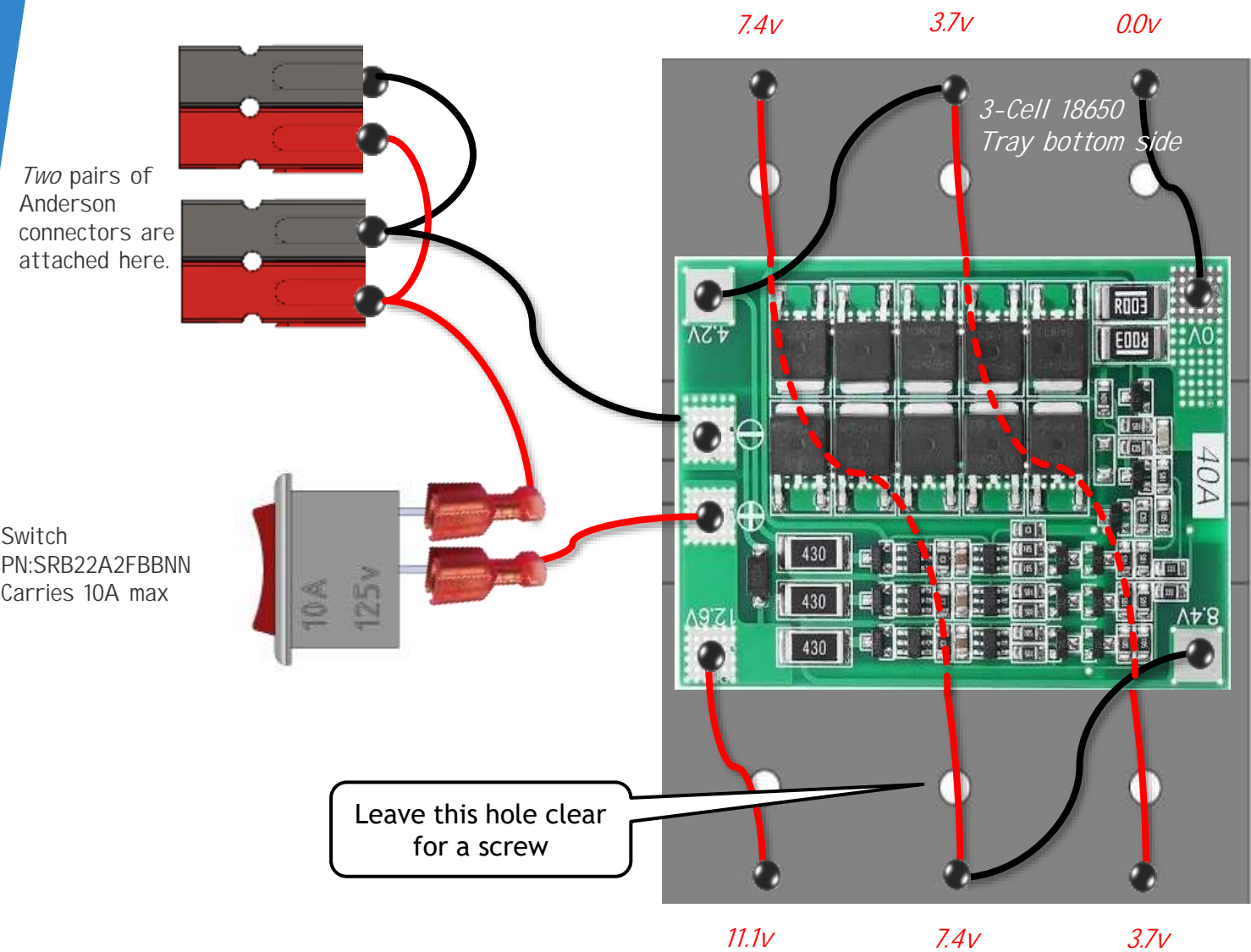


Table of wires to cut (11 total)

Length (mm)
25
56
65
70
90 (qty 2)
25
35 (qty 2)
56
90


LIDAR

Lidar Device




TiM 561

Power Connector Diagram (lidar side)

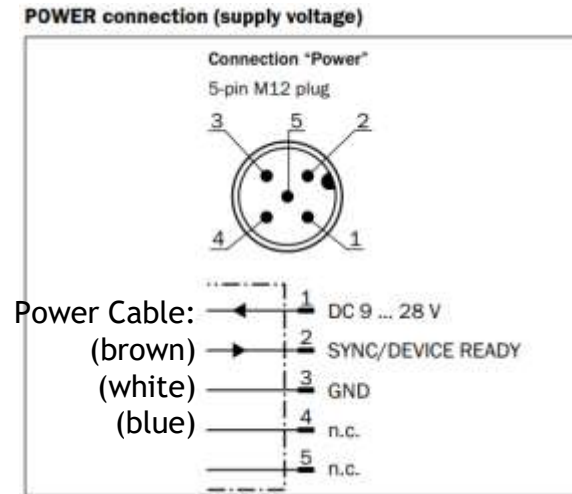

LIDAR-side connector (male pins)

Power Cable Diagram (plugs into lidar)

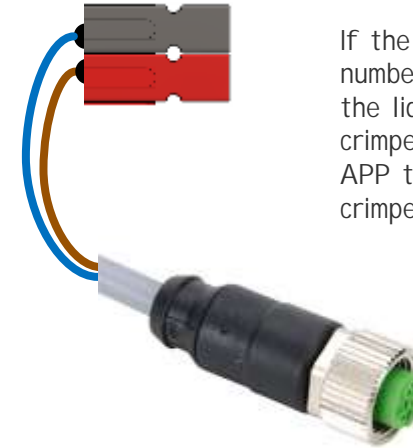

If the indicated cable part number is used for power to the lidar, brown will be crimped into the 12v positive APP terminal and blue is crimped into the negative.


Cable: 7000-12241-2150300

Cable-side connector (female pins)

Typical Lidar power consumption: 2.1w

GamePad

Gamepad Controls Mapping

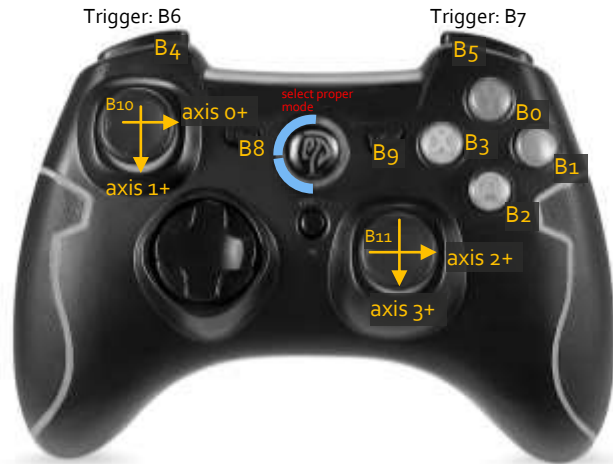

Button Behavior:

- not pressed: 0
- Pressed: 1

Axis behavior:

- Right returns positive values
- down returns positive values
- Outputs:
- Analog axes return values between -1 and 1
- These axes reach their limits before the hard-stop.
- To discover the behavior graphically, visit the html graphical test page [here](#)


Servos

Bridge Power to the LiPo connector




Without a power source available at the positive (third pin) input of the LiPo connector, the board has insufficient current available to the servos to drive servos at full torque or to drive multiple servos.

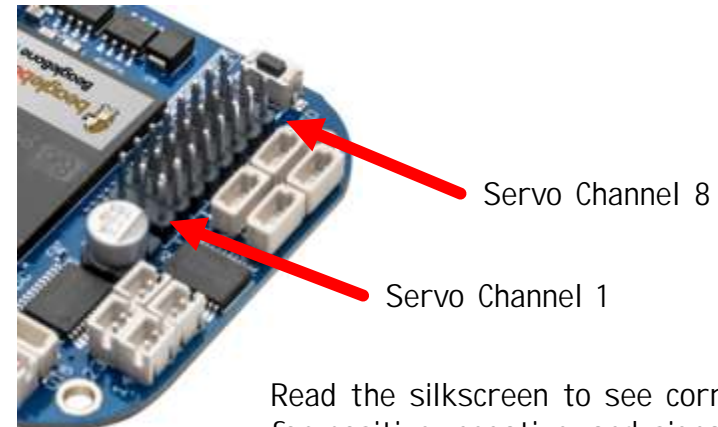A safe fix is to solder the positive terminal of the DC jack to the third pin of the connector shown. When a battery is connected, the pins correspond to 0.0v, 3.7v, and 7.2v terminals of a 2-cell lipo.




RFID reader

RC522 low-cost
RFID Scanner

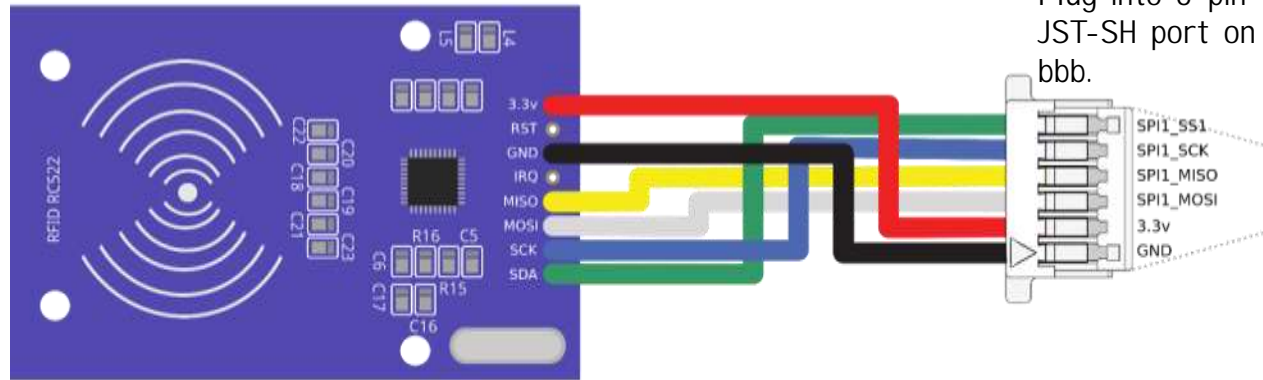

Audio Amp

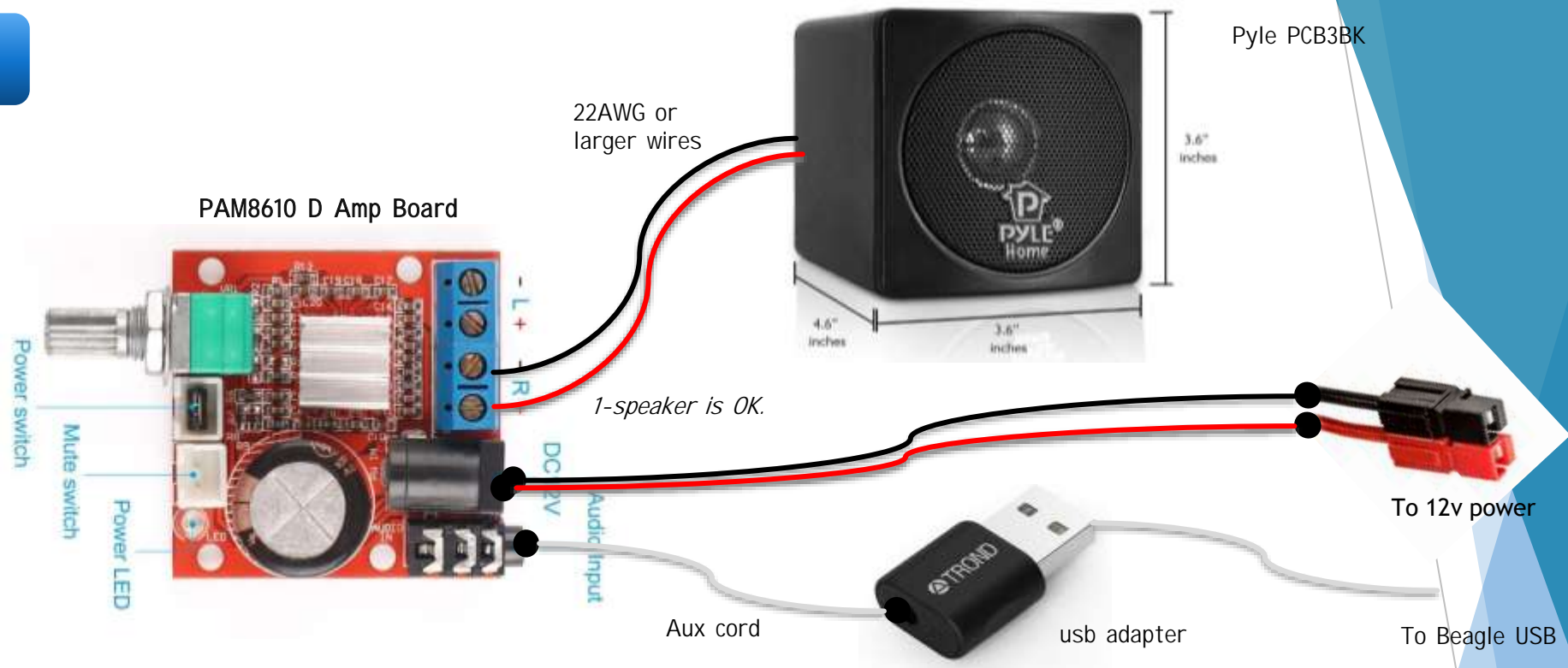

Alternative:


The above setup will support at least 10 watts (this is actually quite loud – easy to hear in a crowded room).

It is also possible to find a speaker which receives BOTH power AND signal over USB. These will be more compact but less powerful. (The speaker shown is 3w max)





GPIO Connections

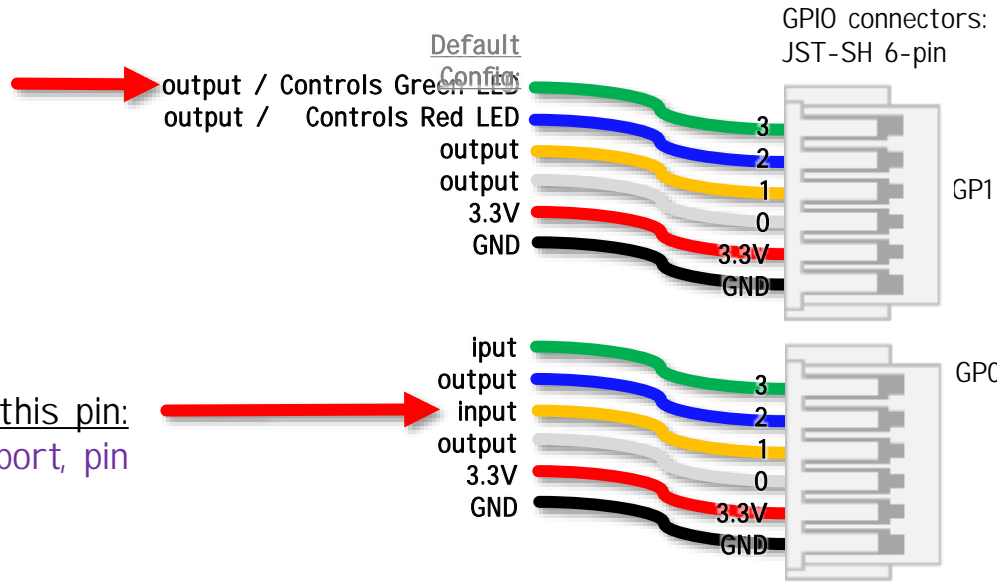Example call for writing to this pin:
`write(1,3,1)` # arguments: port, pin, state



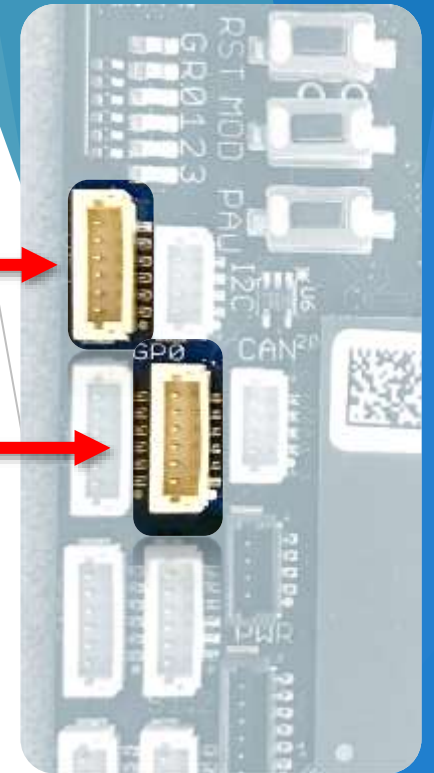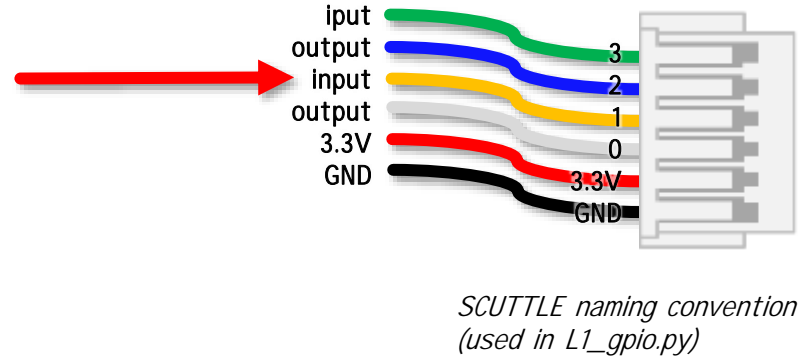Example call for reading this pin:
`read(0, 1)` #arguments: port, pin




Connector vector image
preserved for later use.



Note: JST wires don't come with the proper color sequence. They must be rearranged.

GPIO Example - Relay

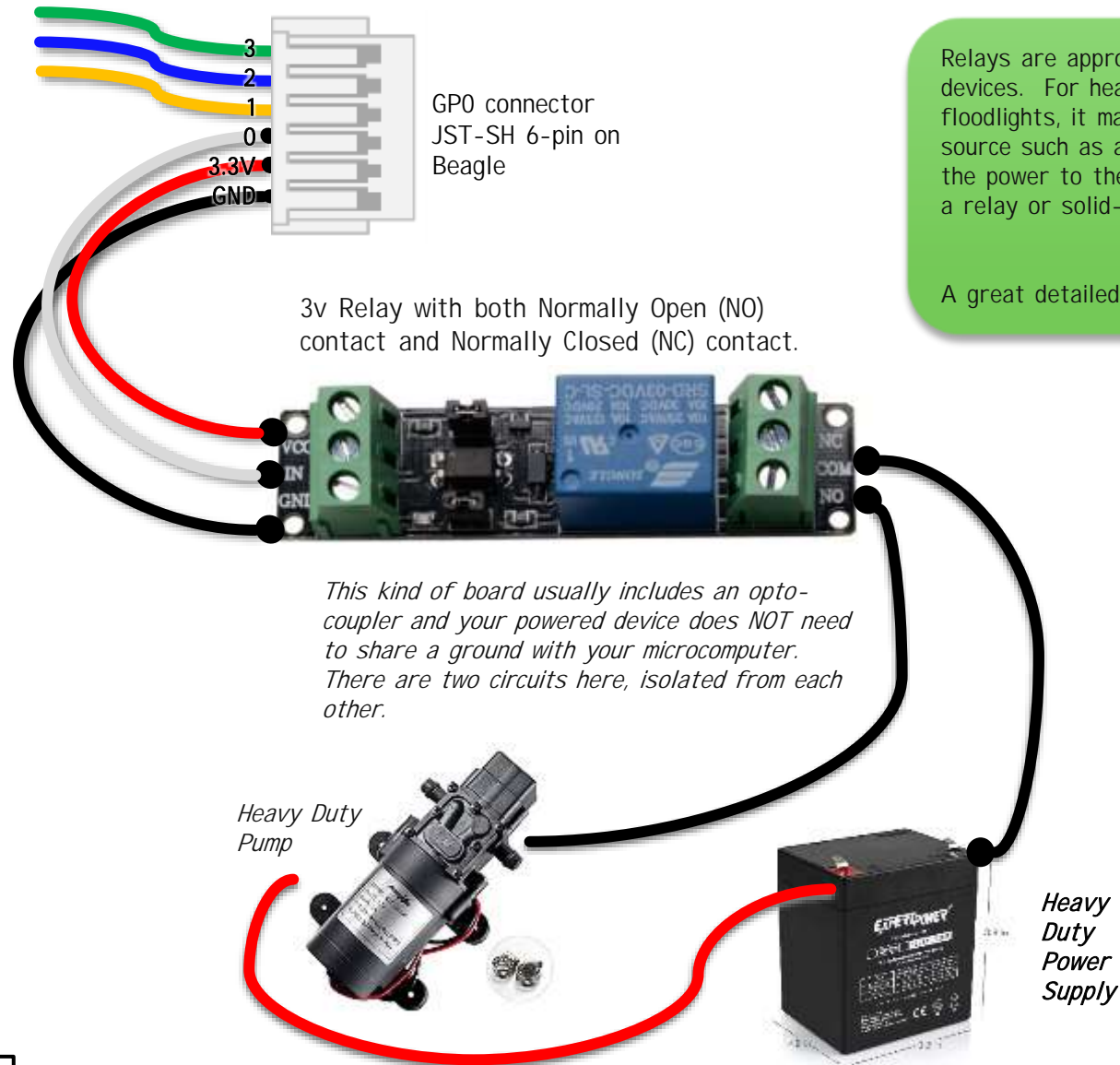

Relays are appropriate for switching of high powered devices. For heavy pumps, motors, fans, or floodlights, it may be best to add a dedicated power source such as an ancilliary battery. Then, control the power to the device using logic-level signals and a relay or solid-state relay.

A great detailed writeup is [here](#).

Twin Relays (tested)

Successfully tested setup 2020.10.10

- Jumper pin is removed from Vcc pins
- Send GND and 5v to the device from Beaglebone PWR
- In our test, the 3.3v from Beagle was insufficient to drive the relays
- Our device was found to be active low although advertised as active high


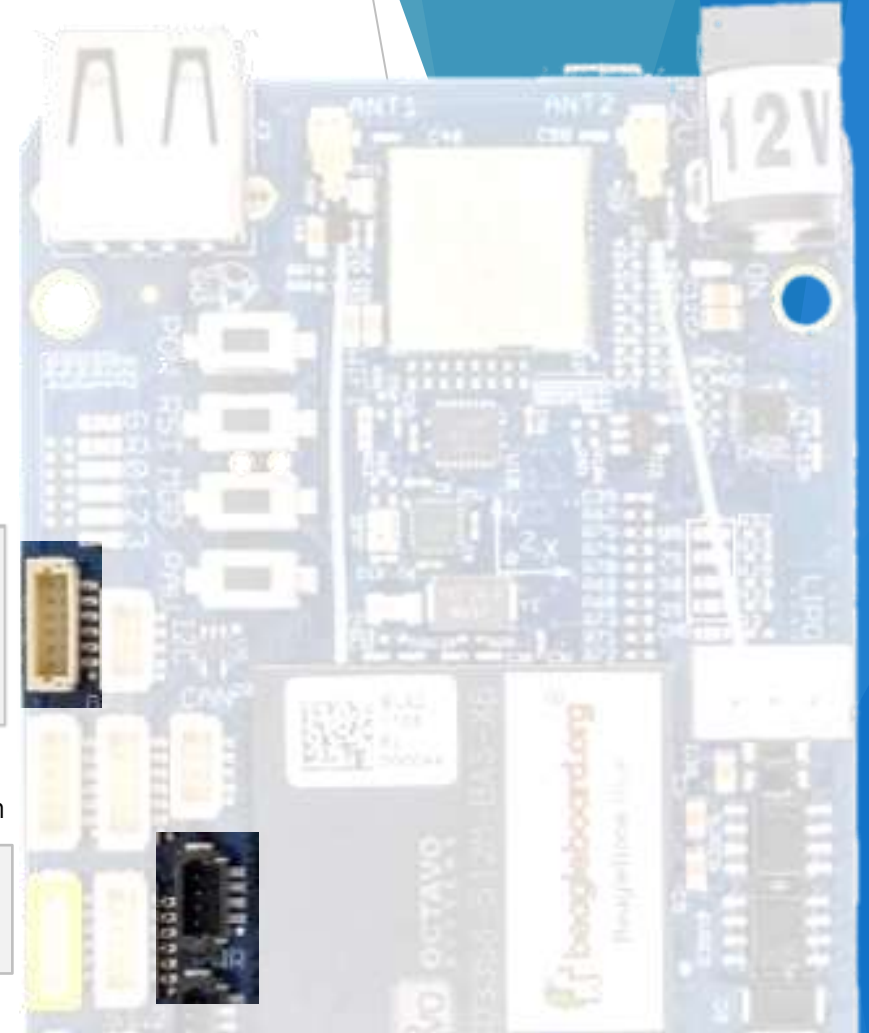


Image credit: Last Minute Engineers ([visit](#))

The problem with active-low relays:

If you have an actuator which must not be actuated until the right moment, (such as a car horn we tested indoors) an active-low device may cause you trouble.

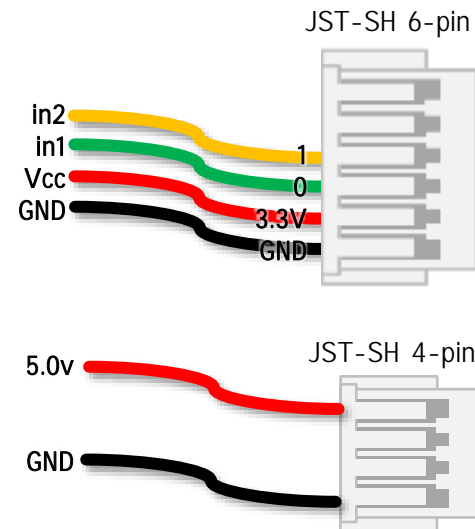Unless the coil power is provided at the exact moment that the signal pin is driven high, there will be an actuation during startup. Consider this when you shop for a relay.




Wifi Antenna

Users can replace the small onboard antenna with their own selected antenna.



SCUTTLE Wire Routing

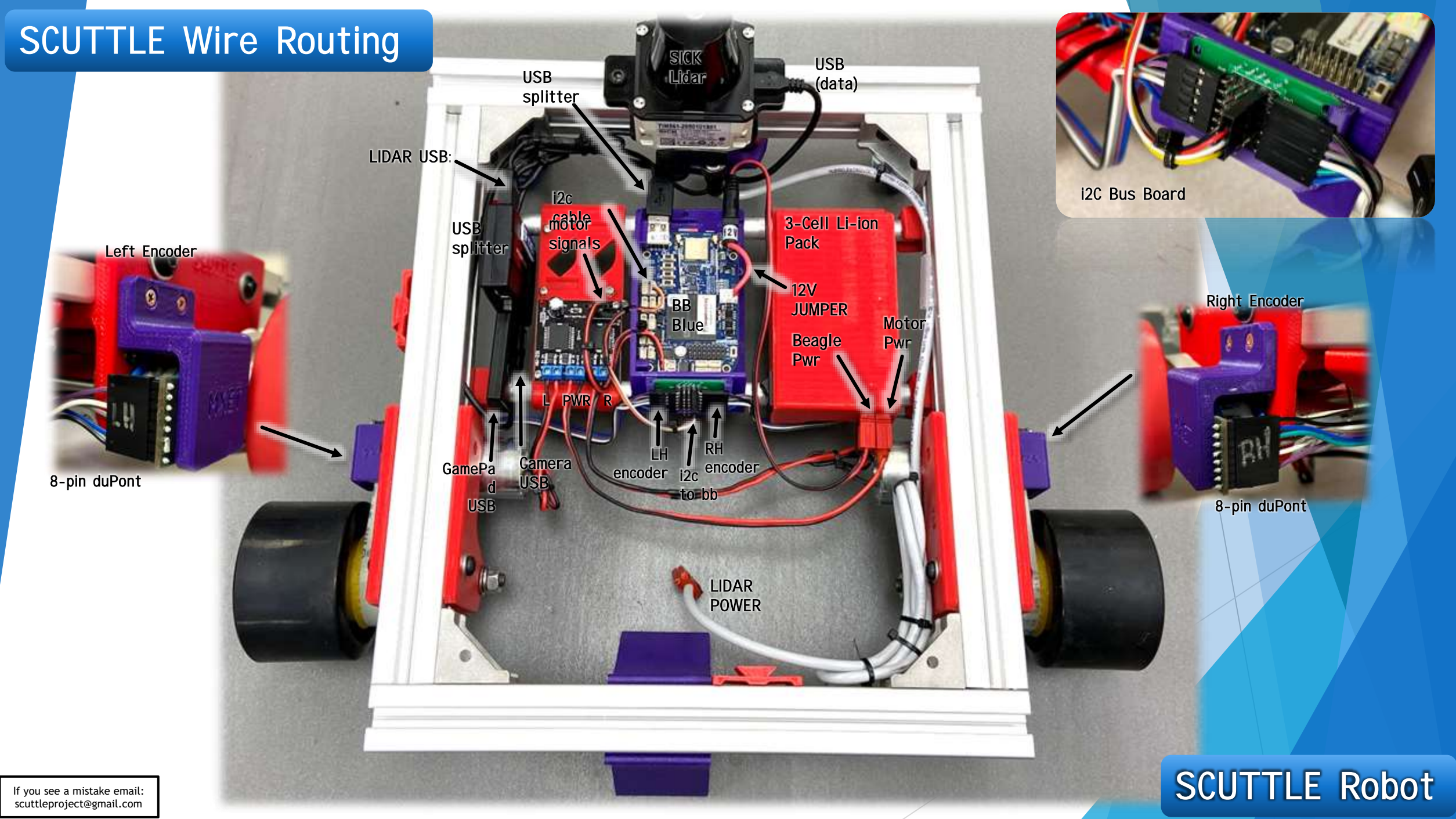

If you see a mistake email:
scuttleproject@gmail.com

SCUTTLE Robot